



Matrix Multiplication Unit

DEVELOPED BY CADEN SANDERS

Project Overview

- ▶ 4 x 4 Matrix Math
 - ▶ Matrix Addition
 - ▶ Matrix Subtraction
 - ▶ Scalar Multiplication
 - ▶ Matrix Multiplication
 - ▶ Matrix Transposition
- ▶ RAM

Project Goals

- ▶ Create a Verilog ecosystem of modules
- ▶ Model basic computer architecture

Assumptions

Memory

- ▶ Modeled after Random Access Memory (RAM)
- ▶ Memory will be volatile SRAM. Data will be stored only while the device has power. Memory will be latched into place and will not need to be “refreshed” to keep an electric charge.
- ▶ reg signed [31:0] Memory [3:0] [255:0]
- ▶ Each element in the memory is a 32-bit integer

CPU

- ▶ The CPU is not independent and will be considered the top-level module.
- ▶ Control signals are sent from a test bench with “initial” procedural blocks for testing and control.
- ▶ Could be connected to an external system that has a functional operating system.

RAM.v	
input wire Clock	
input wire Enable	
input wire ReadWrite	
input wire [9:0] AddressSelect	
input wire signed [31:0] InColumn1	
input wire signed [31:0] InColumn2	
input wire signed [31:0] InColumn3	
input wire signed [31:0] InColumn4	
output reg Done	
output reg signed [31:0] OutColumn1	
output reg signed [31:0] OutColumn2	
output reg signed [31:0] OutColumn3	
output reg signed [31:0] OutColumn4	
reg signed [31:0] Memory [3:0] [255:0]	

Adder.v	
input wire Clock	
input wire [2:0] Operation	
input wire ClearAll	
input wire signed [31:0] ColumnA1	
input wire signed [31:0] ColumnA2	
input wire signed [31:0] ColumnA3	
input wire signed [31:0] ColumnA4	
input wire signed [31:0] ColumnB1	
input wire signed [31:0] ColumnB2	
input wire signed [31:0] ColumnB3	
input wire signed [31:0] ColumnB4	
output reg Error	
output reg Done	
output reg signed [31:0] NewColumn1	
output reg signed [31:0] NewColumn2	
output reg signed [31:0] NewColumn3	
output reg signed [31:0] NewColumn4	


Scalar_Multiplier.v	
input wire Clock	
input wire ClearAll	
input wire Enable	
input wire [2:0] Operation	
input wire signed [31:0] ColumnA1	
input wire signed [31:0] ColumnA2	
input wire signed [31:0] ColumnA3	
input wire signed [31:0] ColumnA4	
input wire signed [31:0] ColumnB1	
input wire signed [31:0] ColumnB2	
input wire signed [31:0] ColumnB3	
input wire signed [31:0] ColumnB4	
output reg Error	
output reg Done	
output reg signed [31:0] NewColumn1	
output reg signed [31:0] NewColumn2	
output reg signed [31:0] NewColumn3	
output reg signed [31:0] NewColumn4	

CPU.v [TOP LEVEL]	
input wire [9:0] Address1	
input wire [9:0] Address2	
input wire [2:0] OperationIn	
input wire Clock	
input wire Reset	
input wire CPUEnable	
input wire ClearAllIn	
input wire [31:0] C*_*	
output reg [31:0] MemoryCounter	
output reg [31:0] MatrixACounter	
output reg [31:0] MatrixBCounter	
output reg ClearAll	
output reg [31:0] AddressSelect	
output reg ReadWrite	
output reg Enable	
output reg Done	
output reg [2:0] State	
output reg signed [31:0] A*_*	
output reg signed [31:0] C*_*	
output reg signed [31:0] DataOut1	
output reg signed [31:0] DataOut2	
output reg signed [31:0] DataOut3	
output reg signed [31:0] DataOut4	
output reg signed [31:0] DataOut5	
output reg signed [31:0] DataOut6	
output reg signed [31:0] DataOut7	
output reg signed [31:0] DataOut8	
output reg signed [31:0] DataInSelector1-4	
reg signed [31:0] MatrixA [3:0] [3:0]	
reg signed [31:0] MatrixB [3:0] [3:0]	
reg [2:0] Operation	
wire Error	
wire Done	
wire signed [31:0] DataIn1	
wire signed [31:0] DataIn2	
wire signed [31:0] DataIn3	
wire signed [31:0] DataIn4	


Subtractor.v	
input wire Clock	
input wire ClearAll	
input wire [2:0] Operation	
input wire signed [31:0] ColumnA1	
input wire signed [31:0] ColumnA2	
input wire signed [31:0] ColumnA3	
input wire signed [31:0] ColumnA4	
input wire signed [31:0] ColumnB1	
input wire signed [31:0] ColumnB2	
input wire signed [31:0] ColumnB3	
input wire signed [31:0] ColumnB4	
output reg Error	
output reg Done	
output reg signed [31:0] NewColumn1	
output reg signed [31:0] NewColumn2	
output reg signed [31:0] NewColumn3	
output reg signed [31:0] NewColumn4	

Matrix_Multiplier.v	
input wire Clock	
input wire ClearAll	
input wire Enable	
input wire [2:0] Operation	
input wire signed [31:0] ColumnA1	
input wire signed [31:0] ColumnA2	
input wire signed [31:0] ColumnA3	
input wire signed [31:0] ColumnA4	
input wire signed [31:0] RowB1	
input wire signed [31:0] RowB2	
input wire signed [31:0] RowB3	
input wire signed [31:0] RowB4	
output reg Error	
output reg Done	
output reg signed [31:0] Result	


Transposition.v	
input wire Clock	
input wire ClearAll	
input wire Enable	
input wire [2:0] Operation	
input wire signed [31:0] Column1	
input wire signed [31:0] Column2	
input wire signed [31:0] Column3	
input wire signed [31:0] Column4	
output reg Error	
output reg Done	
output reg signed [31:0] NewRow1	
output reg signed [31:0] NewRow2	
output reg signed [31:0] NewRow3	
output reg signed [31:0] NewRow4	

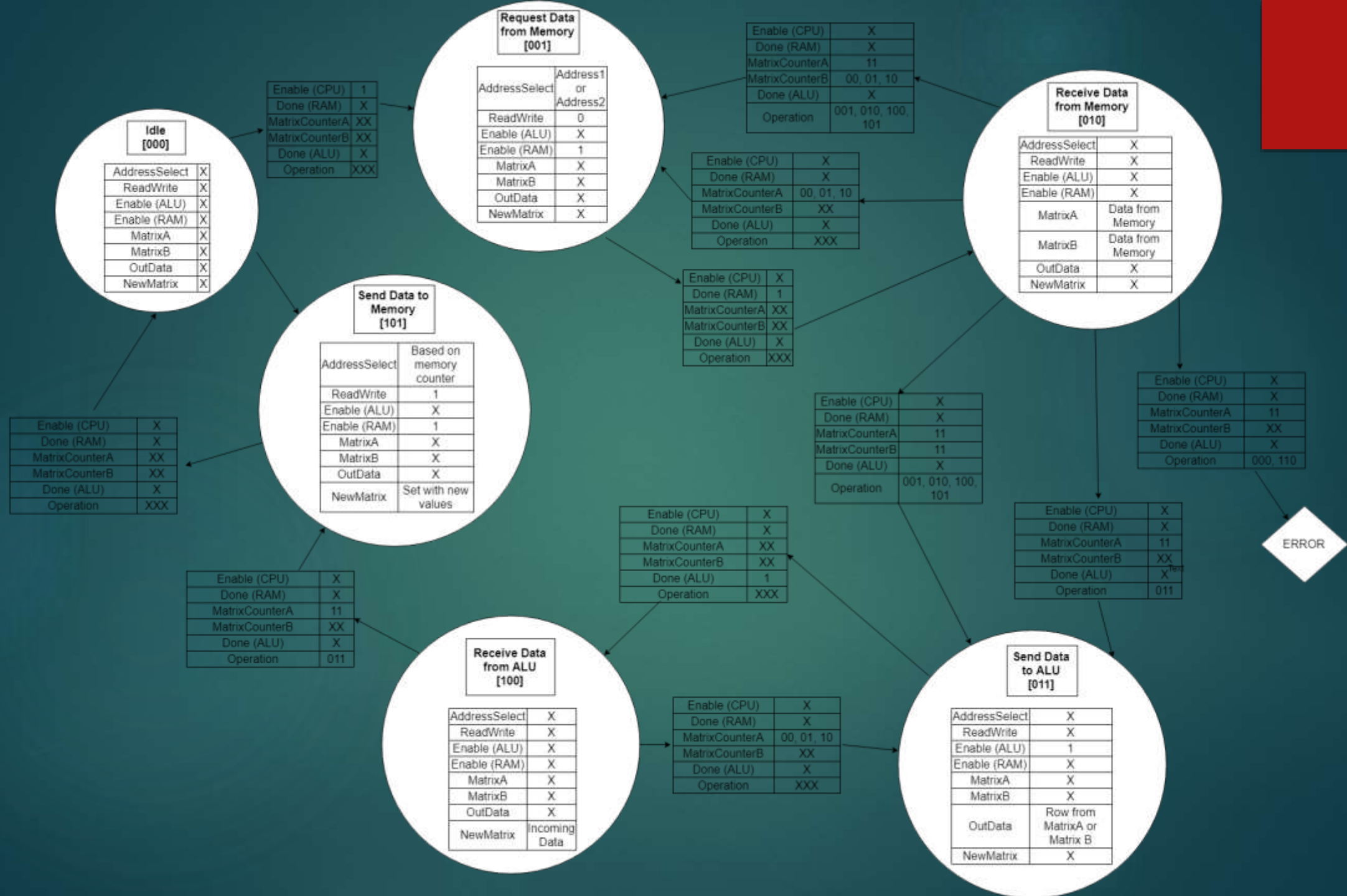


Development Environment

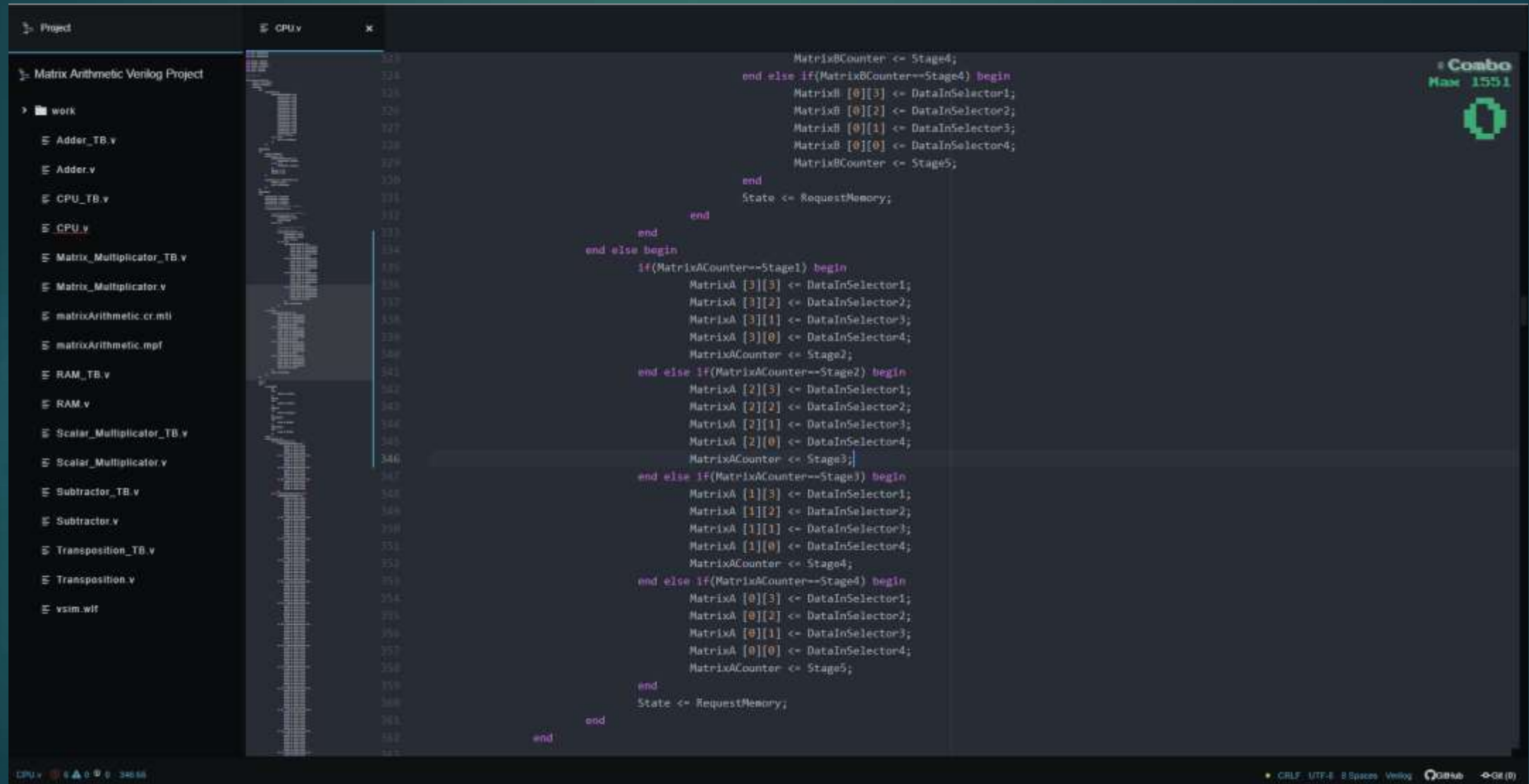

Addition

 


CPU Memory Addressing

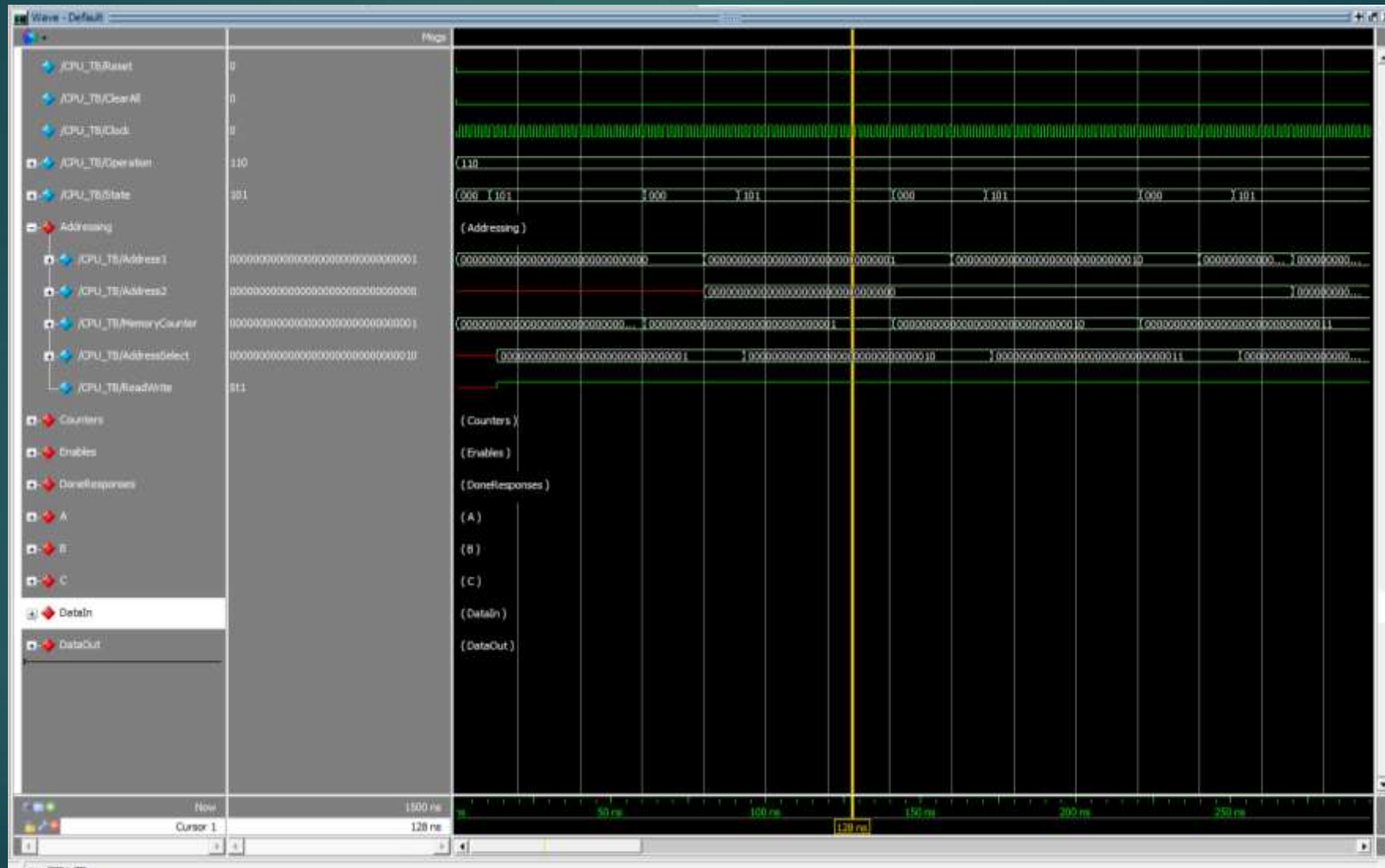


ALU Enables and Done Responses




Loading CPU Registers from Memory

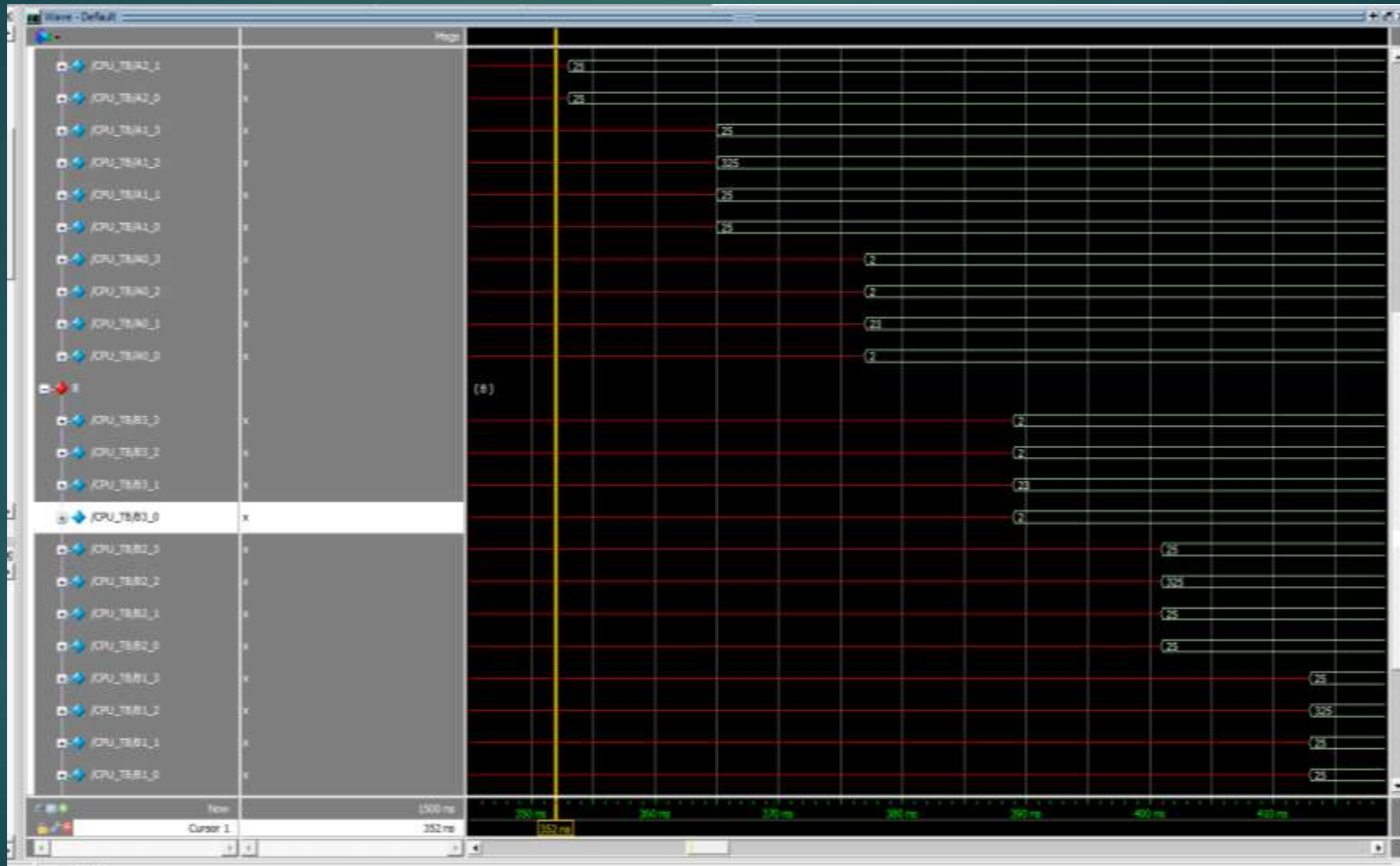


Matrix Multiplication

 


Scalar Multiplication

 

Subtraction

 

Transposition

 



Questions?